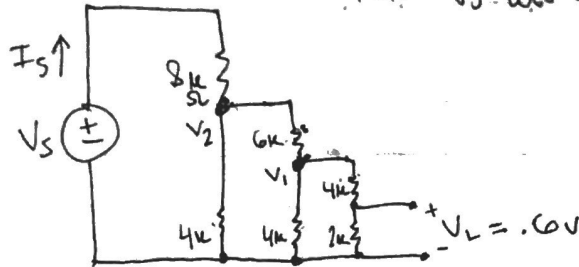


ECEN 325

# HW #1

1) a)

Find  $V_s$  and  $I_s$



$$0.6V = \frac{2k}{4k+2k} V_1 \quad \# \quad V_1 = 1.8V$$

$$1.8V = \frac{4k}{4k+6k} V_2$$

$$V_2 = 4.5V$$



$$V_2 = 6.3V$$

$$1.8V = \frac{4k \parallel (4k+2k)}{(4k \parallel 4k+2k) + 6k} V_2$$

$$6.3V = \frac{V_s}{8k + (4k \parallel 6k) \parallel (4k \parallel 4k+2k)}$$

$$4.5V = \frac{4k}{8k+4k} V_s$$

$$V_s = 24.9V$$

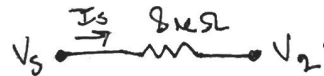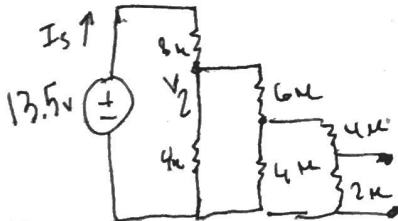


$$V_s = 13.5V$$

$$V_2 = 4.5V$$

$$V_2 = 6.3V$$

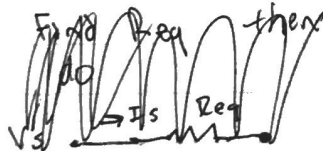
$$I_s = \frac{24.9V - 6.3V}{8000\Omega}$$



$$I_s = 1.25mA$$

$$I_s = 2.325mA$$

17b)

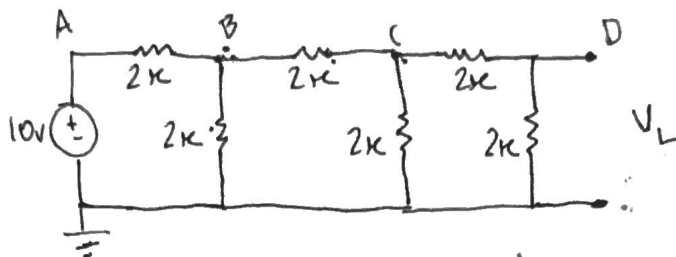

$$V_B = \frac{2k}{2k+2k} \cdot 10V$$

$$V_B = 5V$$

$$V_B = 2.22V$$

$$V_B = 3.846V$$

$$V_B = \frac{10 \cdot (2k \parallel (2k \parallel (2k \parallel 4k)))}{2k + (2k \parallel (2k \parallel (2k \parallel 4k)))}$$

$$V_C = \frac{2k}{2k+2k} \cdot 5V$$

$$V_C = 2.5V$$

$$V_C = 1.5384V$$

$$V_C = \frac{3.846V \cdot (2k \parallel (2k \parallel 4k))}{2k + (2k \parallel (2k \parallel 4k))}$$

$$V_L = V_D = \frac{2k}{2k+2k} \cdot 2.5V$$


$$V_L = 769mV$$

$$V_L = \frac{2k}{4k} \cdot 1.5384$$

$$V_L = 1.25V$$

$$I_L = 1.25V / 200\Omega = 6.25mA$$

$$I_L = 4.16mA$$

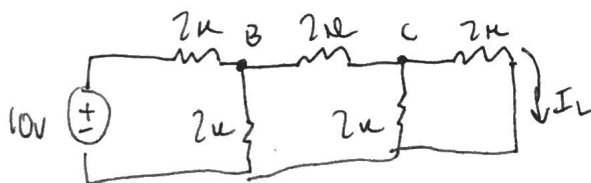



$$V_B = 10 \cdot \frac{2k \parallel (2k + 1k)}{2k + (2k \parallel (2k + 1k))}$$

$$V_B = 3.75V$$

$$V_C = 3.75 \cdot \frac{2k \parallel 1k}{1k + 2k}$$


$$V_C = 1.25V$$

$$\frac{1.25}{2k} = 6.25E-4 A$$

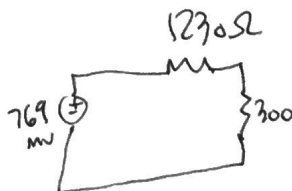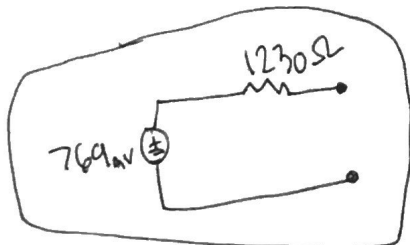

$$I_L = \frac{769mV}{1230\Omega + 300\Omega} = 5.026E-4 A$$
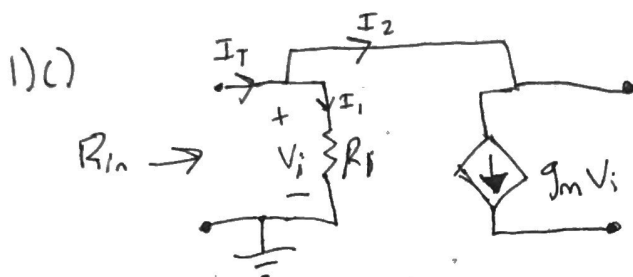
$$I_L = \frac{769mV}{1230\Omega + 300\Omega} = 5.026E-4 A$$



$$I_1 = \frac{V_i}{R_i}$$

$$I_T = I_1 + I_2$$

$$I_T = \frac{V_i}{R_i} + g_m V_i$$

$$I_T = V_i \left( \frac{1}{R_i} + g_m \right)$$

$$\frac{V_i}{I_T} = \frac{V_i}{V_i \left( \frac{1}{R_i} + g_m \right)}$$

$$R_{in} = \frac{R_i}{1 + R_i g_m}$$

2)  $\text{gain} = \frac{V_{out}}{V_{in}} \quad \text{db} = 20 \log_{10} \left( \frac{\omega}{\omega_c} \right)$


$$\phi = -\tan^{-1} \left( \frac{\omega}{\omega_c} \right)$$

Standard form of the transfer function,  $H(\omega)$ , is where the terms  $\omega$  are written such that the ~~real~~ ~~part~~ imaginary part is written as the reciprocal of an angular frequency ( $\omega_z$  or  $\omega_p$ )

Transfer function is comprised of  $H(\omega) = M(\omega) e^{j\phi(\omega)}$  which is magnitude,  $M(\omega)$ , and phase angle  $\phi(\omega)$

$$H_1(s) = \frac{30(10+s)}{(200+2s)(1000+2s)}$$
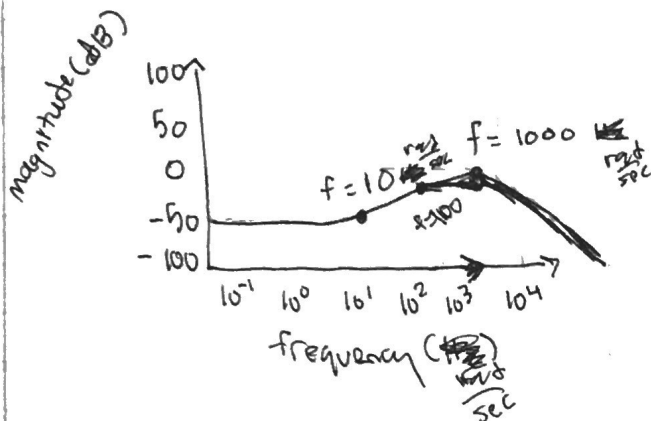
$$= .003 \frac{(\frac{s}{10} + 1)}{(\frac{s}{100} + 1)(\frac{s}{1000} + 1)}$$




$$= .003 \frac{(\frac{s}{10} + 1)}{(\frac{s}{100} + 1)(\frac{s}{1000} + 1)}$$

Constant = .003 = -50 dB

Poles = -100, -1000

Zero = -10

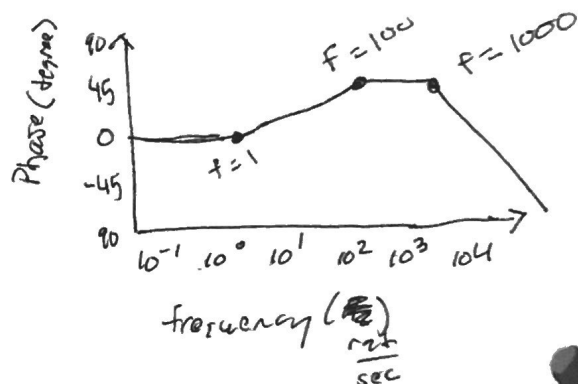



$$H_2(s) = 400 \frac{(6s+60)}{(2s+4)(26+100)(4s+400)}$$

$$= \frac{400 \cdot 10}{2 \cdot 50 \cdot 100} \frac{(\frac{s}{10} + 1)}{(\frac{s}{2} + 1)(\frac{s}{50} + 1)(\frac{s}{100} + 1)}$$

Constant = .4 = -8 dB


Poles = -2, -50, -100

Zero = -10

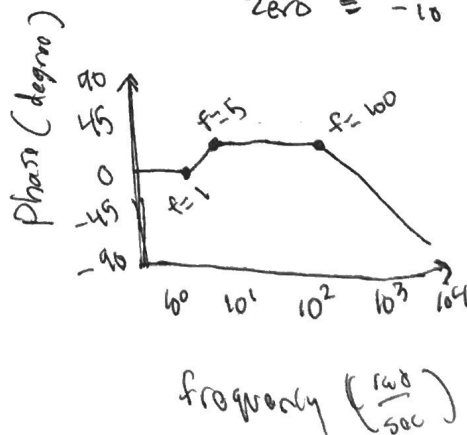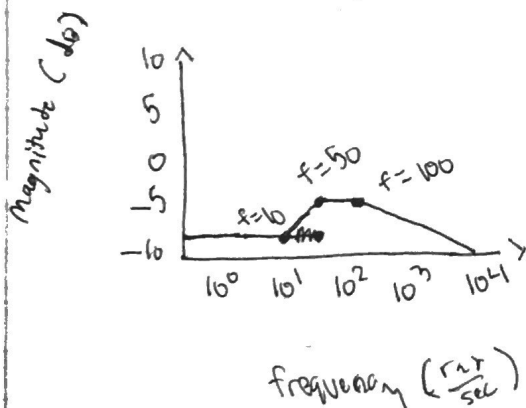


$$H_2(s) = 8 \frac{10 + 10s}{s(s^2 + 4s + 16)} = 8 \cdot \frac{1}{16} \frac{\left(\frac{s}{1} + 1\right)}{s\left(\frac{s^2}{16} + \frac{s}{4} + 1\right)} = .5 \frac{\frac{s}{1} + 1}{s\left(\frac{s^2}{16} + \frac{s}{4} + 1\right)}$$

Magnitude (dB)

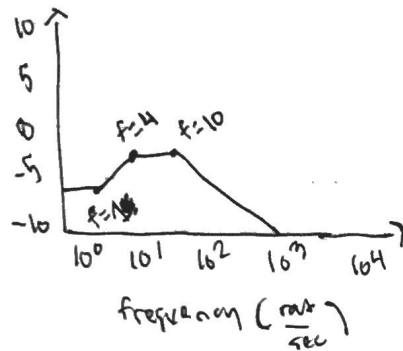

Phase (degree)

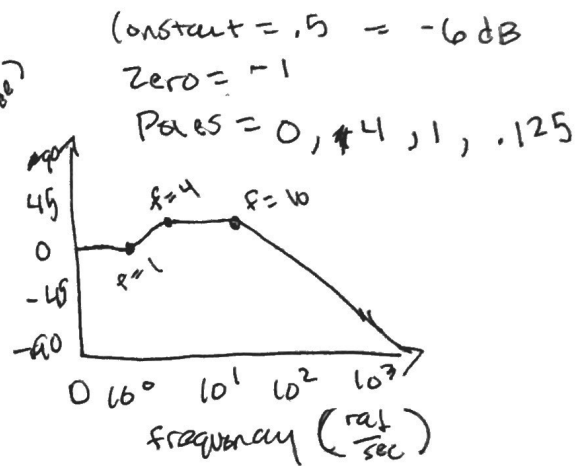


(constant = .5 = -6 dB)

Zero = -1

Poles = 0, 4, 1, .125

3) a)

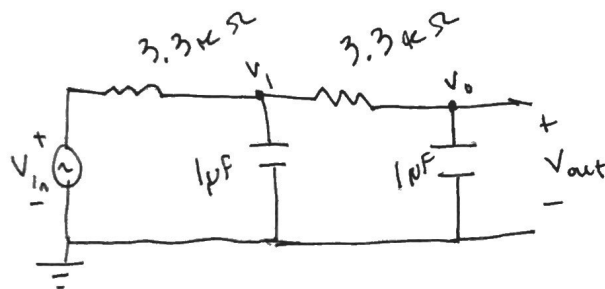

$$\frac{V_1 - V_{in}}{R_1} + \frac{V_1}{sC_1} + \frac{V_1}{R_2 + sC_2} = 0$$

$$V_1 \left[ \frac{1}{R_1} + sC_1 + \frac{sC_2}{R_2 sC_2 + 1} \right] = \frac{V_{in}}{R_1}$$

$$V_1 [1 + sC_2 R_2 + R_1 R_2 s^2 C_1 C_2 + sC_1 R_1 + sC_2 R_1] = V_{in} [1 + sC_2 R_2]$$

$$V_1 [s^2 C_1 R_2 R_1 + s [C_2 R_2 + C_1 R_1 + C_2 R_1] + 1] = V_{in} [1 + sC_2 R_2]$$

$$V_{out} = \frac{V_1}{R_2 sC_2 + 1} = \frac{V_{in}}{s^2 C_1 R_2 R_1 + s [C_2 R_2 + C_1 R_1 + C_2 R_1] + 1}$$



~~H(s) =~~

$$\frac{91827.365}{(s + 4.95E-3)^2 + (0.999)^2}$$

$$\frac{91827.365}{(s + 4.95E-3)^2 + (0.999)^2}$$

$$H(s) = \frac{91827.365}{(s + 4.95E-3)^2 + (0.999)^2}$$

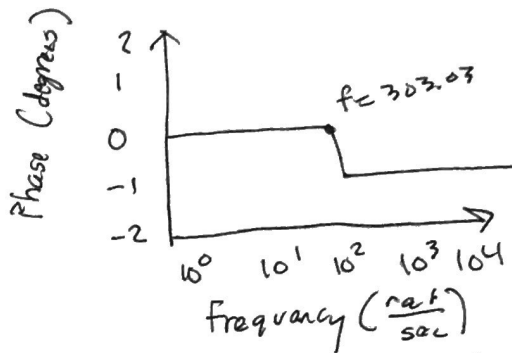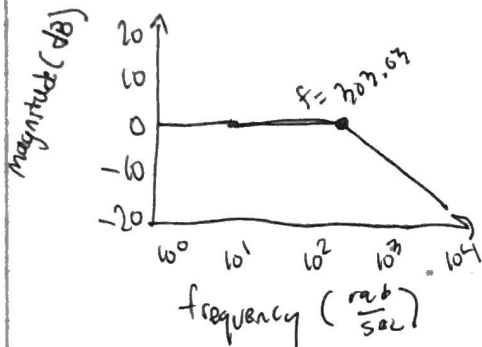$\text{pole} = 307.07 \text{ rad/sec}$   
 $\text{constant} = 0 \text{ dB}$




$$\text{gain} = \frac{|V_o|}{|V_{in}|} = \frac{1/C^2 R^2}{s^2 + s \frac{C_1 C R D}{C^2 R^2} + \frac{1}{C^2 R^2}}$$

gain = 1  
(at  $\omega = 0$ )

gain = 0  
(at  $\omega = \infty$ )

low pass

b)

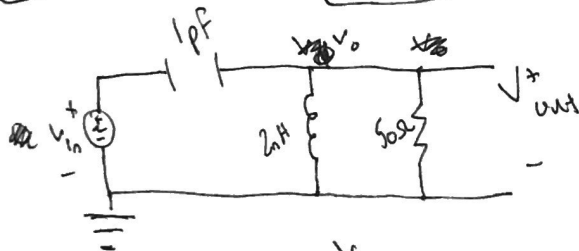



$$\frac{V_i}{sL} + \frac{V_o}{R} + \frac{V_o - V_{in}}{sC} = 0$$

$$V_o \left[ \frac{1}{sL} + \frac{1}{R} + sC \right] = V_{in} \cdot sC$$

$$V_o [R + sL + s^2 LCR] = V_{in} [s^2 RLC]$$

$$H(s) = \frac{s^2}{s^2 + s(2\pi \times 10^3) + 5 \times 10^6}$$

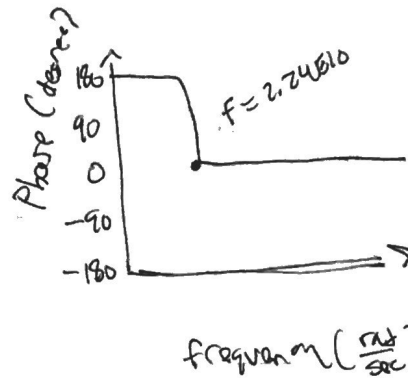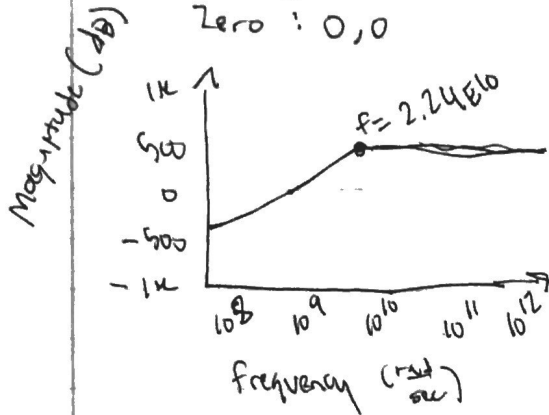pole:  $2.24 \times 10$   
 Constant:  $-413 \text{ dB}$   
 Zero:  $0, 0$




$$\frac{s^2}{s^2 + (2.24 \times 10)s + 5 \times 10^20}$$

High Pass

- ①  $s=0$  gain = 0
- ②  $s=\infty$  gain = 1

(c)

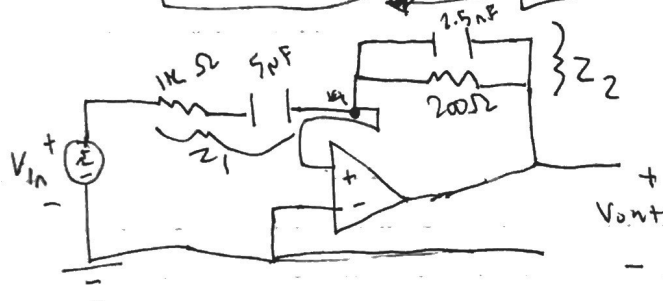

$$\frac{0 - V_{in}}{Z_1} + \frac{0 - V_o}{Z_2} = 0$$

$$\frac{V_o}{V_{in}} = \frac{-Z_2}{Z_1}$$

$$Z_1 = R_1 + \frac{1}{sC_1}$$

$$Z_2 = \frac{200}{5 \times 10^{-6}s + 1}$$

$$\frac{V_o}{V_{in}} = - \frac{200}{(5 \times 10^{-6}s + 1) \left( R_1 + \frac{1}{sC_1} \right)}$$



$$= \frac{-0.01s}{\left( 1 + \frac{s}{200} \right) \left( 1 + \frac{s}{2 \times 10^5} \right)}$$

Magnitude (dB)

Constant = -40 dB

Zero = -100

Pole = -200, -255

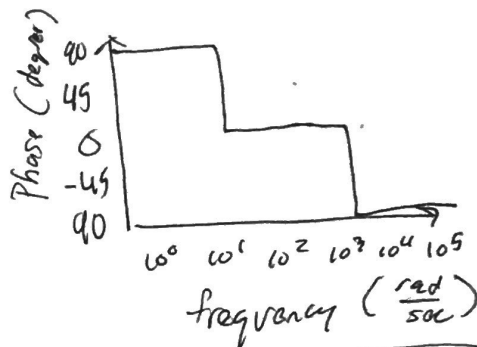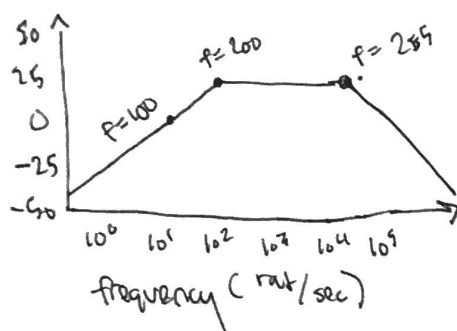

$$\frac{-0.15}{(1 + \frac{s}{200})(1 + \frac{s}{2000})}$$

gain @  $s=0 = 0$   
 gain @  $s=\infty = 0$   
 band pass filter

4)

In industry, they use bode plots, specifically frequency domain to design and analyze analog filters to be used in closed-loop systems. A common purpose would be in a power supply. This product requires great stability so close attention needs to be on the design and analysis of a filter. ~~they use not only bode plots but also~~ ~~at graphing~~ ~~they~~ they test the system at several frequencies just like our bode plots, and analyze the resulting output that comes out of their system. This is similar to our bode plots. They analyze the difference in gain and phase shifting. They look at cross over frequency, phase margin, and gain margin, these give more insight into the stability of the system.